PID MOTOR CONTROL LOOP

Jason Gallicchio and Claude, rev A, 2026-10-24

LAB 10L: a PID loop holds a fader (motorized potentiometer) where TARGET says.

POWER: +15 V, GND, −15 V on the POWER terminal, 1 A per rail.
    Both green lamps light. A reversed supply is blocked: the lamps stay dark.
FADER (Bourns PSM01-082A-103B2): motor A to MOTOR, motor B to GND.
    Track 1, 2, 3 to POT 1 (+), 2 (wiper), 3 (−): the numbers match.
    Check with LOOP open: slide it by hand, POSITION is +7.7 V at the + end.
    LOOP closed and the slider runs to an end and stays: swap the motor leads.
INPUTS
    TARGET knob: centre detent = 0 V, clockwise +, up to +/−6.4 V.
    TARGET IN jack: a function generator, +/−12 V max.
        Try +/−3 V: a 0.2 Hz square wave for steps, a 0.05 Hz triangle for stick-slip.
OUTPUTS, each through 1k: for a scope, not a load
    POSITION OUT: the fader's wiper, buffered. DRIVE OUT: the motor drive.
SWITCHES
    TARGET SOURCE 1 = the knob
                   3 = the TARGET IN jack
    LOOP   1 = open: no feedback; DRIVE = P GAIN x TARGET (+ D, I if on)
                       P GAIN anticlockwise, D and I off: DRIVE = TARGET
                   3 = closed: POSITION fed back, the loop holds TARGET
    D IN / OFF   1 = off: the differentiator's output shorted
                   3 = D into the sum
    D CAPACITOR   1 = 22 nF, for this fader
                   3 = 100 nF, for the book's slower rotary pot
    I IN / OFF   1 = off: the 1 uF shorted, so I restarts from zero
                   3 = I into the sum
TRIMMERS: clockwise = more resistance: more P, more D, but LESS I.
START: every switch on 1. P and D GAIN anticlockwise, I GAIN clockwise.
    LOOP to 3: the slider follows the knob. Raise P GAIN until it rings.
    D IN, raise D GAIN: the ringing dies. Lower P; I IN: the error goes to 0.
WARNINGS
    A stall at full drive or a short to GND opens the fuse (red lamps): it resets.
    A stall at a few volts does not: HOT copper reaches 90 C, so use the standoffs.
    Never short MOTOR or DRIVE to a rail. Power off to wire the fader.

https://github.com/gallicchio/motor-pid
circuit, scripts, schematic, this board

Sheet:		
File: motorpid.kicad_pcb		
Title:		
Size: A4	Date:	**Rev:**
KiCad E.D.A. 10.0.7		Id: 1/1